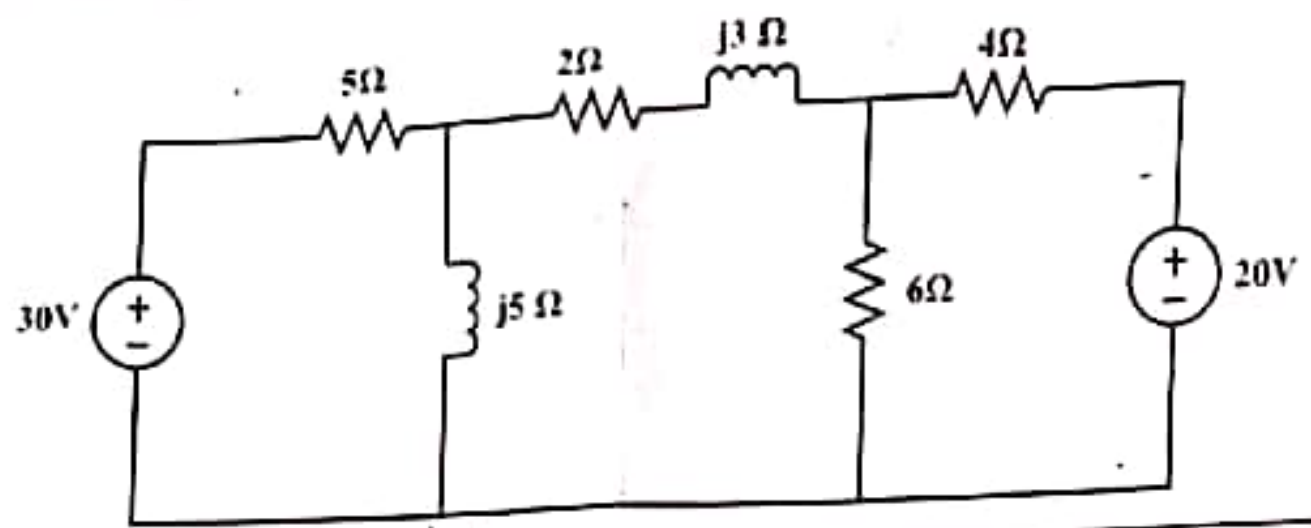
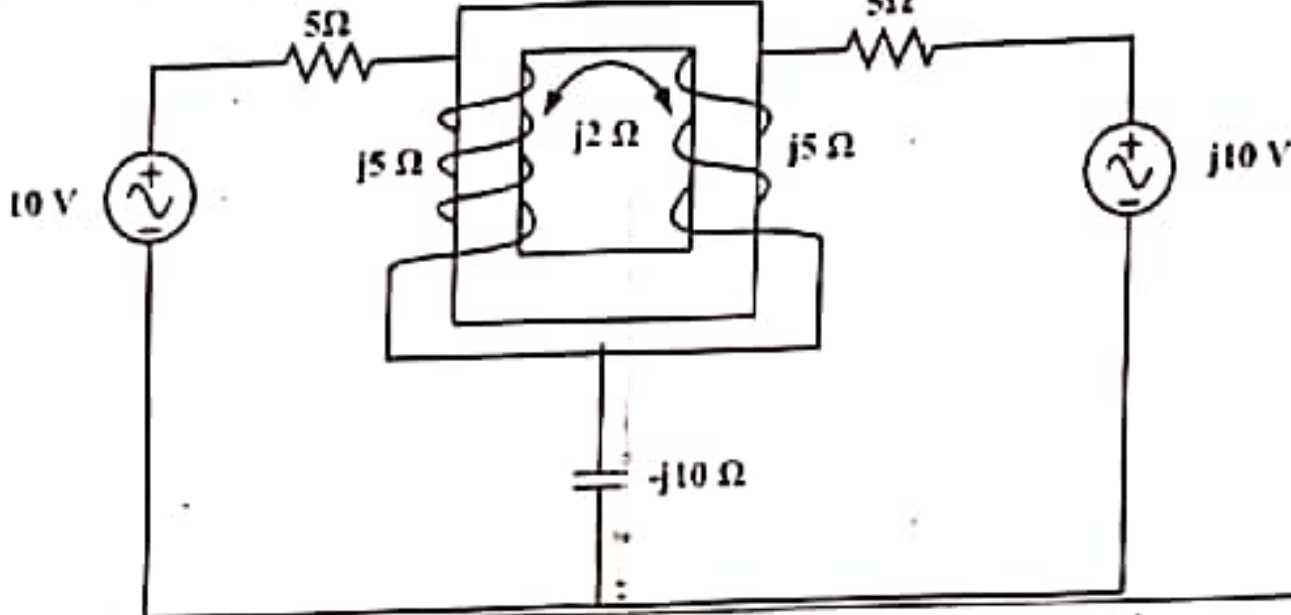
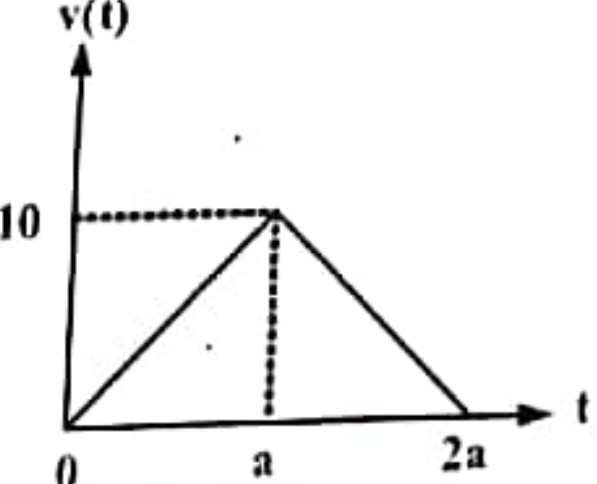
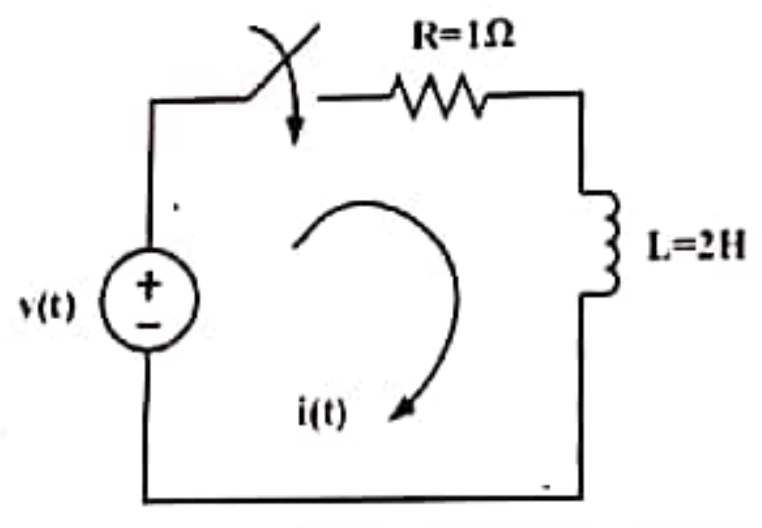
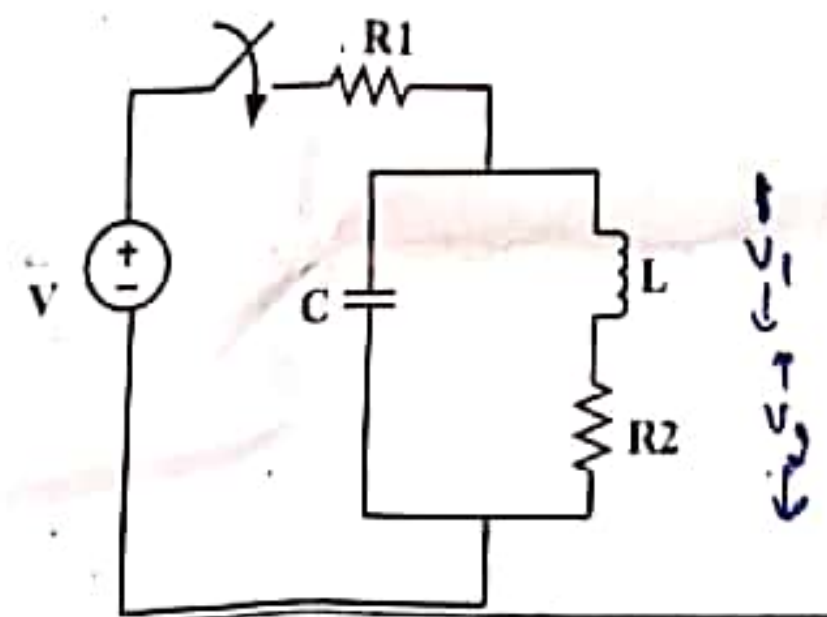


Name of the Student Scholar No:
MAULANA AZAD NATIONAL INSTITUTE OF TECHNOLOGY BHOPAL
DEPARTMENT OF ELECTRICAL ENGINEERING
 Mid Term Exam-SEPT 2023

Course: B.Tech
 Subject Name: Network Analysis
 Duration: 1.5 Hours

Semester: III
 Subject Code: EE-213
 Maximum Marks: 20

Q.1	Find the current through $(2+j3) \Omega$ impedance using superposition theorem 	5
Q.2	Obtain the dotted equivalent circuit for the shown coupled circuit and use it to find the voltage across the $(-j10 \Omega)$ reactance. 	5
Q.3	The switch is closed at time $t=0$ and voltage $v(t)$ is applied across the network. Find $i(t)$ using Laplace Transform.  	5
Q.4	In the shown network, the switch is closed at $t=0$, with zero capacitor voltage and inductor current. Find v_1, v_2 at $t=0^+$ and v_1, v_2 at $t=\infty$. 	5

Course Coordinator: Dr. Savita Nema