

MAULANA AZAD NATIONAL INSTITUTE OF TECHNOLOGY, BHOPAL

Department of Electrical Engineering

B. Tech. IV Semester

Sub: Electronics Devices & Circuits (EE-223)

Assignment - 1

Submission deadline: 27.03.2025

- Q.1.** A voltage amplifier of the type of Fig. 1.1 is fed by a 200-mV source and drives a $10\ \Omega$ load. Voltmeter measurements give $v_I = 150\ \text{mV}$ and $v_O = 10\ \text{V}$. If disconnecting the load causes v_O to rise to $12\ \text{V}$, and then connecting a $30\text{-k}\Omega$ resistor across the input-port terminals causes v_O to drop from $12\ \text{V}$ to $9.6\ \text{V}$, find R_s , R_i , A_{oc} , and R_o .

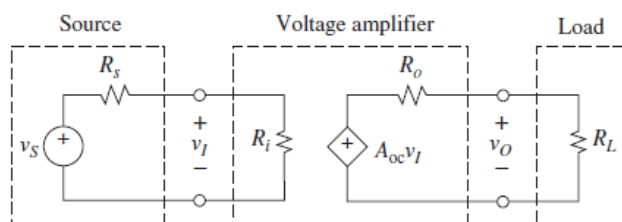


Fig. 1

- Q.2.** In Ltspice simulation platform, obtain the Input Offset Current, Input bias current, Input & Output Offset Voltage the Bandwidth, Slew Rate & Output Impedance of an operational Amplifier OP191.
- Q.3.** Design a noninverting amplifier whose gain is variable over the range $0.5\ \text{V/V} \leq A \leq 5\ \text{V/V}$ by means of a $100\text{-k}\Omega$ pot. Validate the designed non-inverting amplifier in Ltspice simulation platform.
- Q.4.** A source $v_s = 2\ \text{V}$ with $R_s = 10\ \text{k}\Omega$ is to drive a gain-of-five inverting amplifier implemented with $R_1 = 20\ \text{k}\Omega$ and $R_f = 100\ \text{k}\Omega$. Find the amplifier output voltage and verify that because of loading its magnitude is less than $2 \times 5 = 10\ \text{V}$. (b) Find the value to which R_f must be changed if we want to compensate for loading and obtain a full output magnitude of $10\ \text{V}$. Validate the result in Ltspice simulation platform.
- Q.5.** Find v_N , v_P , and v_O in the circuit of Fig. 2, as well as the power released by the 4-V source. Validate the result in Ltspice simulation platform.

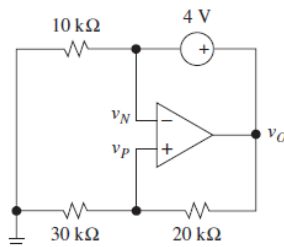


Fig. 2

- Q.6.** The audio panpot circuit of Fig. 3 is used to continuously vary the position of signal v_I between the left and the right stereo channels. (a) Discuss circuit operation. (b) Design R_1 and R_2 so that $v_L/v_I = -1\ \text{V/V}$ when the wiper is fully down, $v_R/v_I = -1\ \text{V/V}$ when the wiper is fully up, and $v_L/v_I = v_R/v_I = -1/\sqrt{2}$ when the wiper is halfway. Validate the design in Ltspice simulation platform.

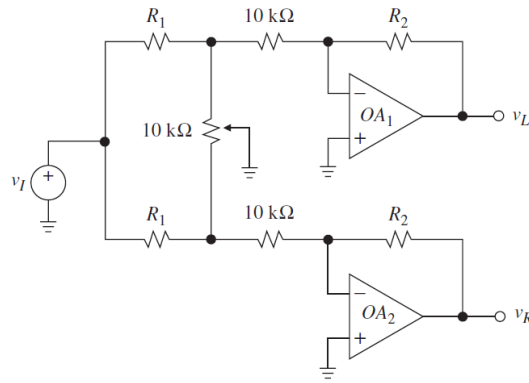


Fig. 3

- Q.7.** In the differentiator circuit based on Op-amp, let $C = 10 \text{ nF}$ and $R = 100 \text{ k}\Omega$, and let v_I be a periodic signal alternating between -2 V and 2 V with a frequency of 100kHz . Simulate and plot v_I and v_O versus time, if v_I is (a) a sine wave; (b) a triangular wave.
- Q.8.** In the integrator of Fig. 1.20 let $R = 100 \text{ k}\Omega$ and $C = 10 \text{ nF}$. Simulate and plot $v_I(t)$ and $v_O(t)$ if $v_I = 5 \sin(2\pi 100t) \text{ V}$.
- Q.9.** An OP AMP circuit is shown in the Fig. 4 below:

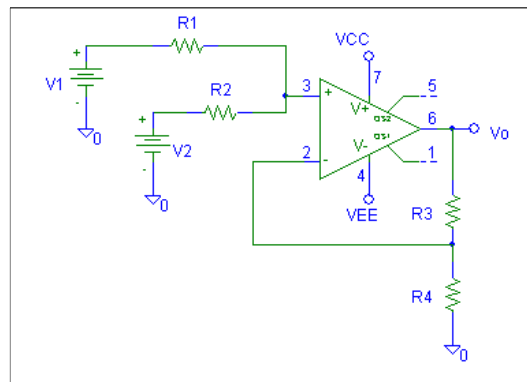


Fig. 4

Prove that the output is

$$V_O = \frac{1}{2} \times \left(1 + \frac{R_3}{R_4} \right) \times (V_1 + V_2)$$

If $R_1 = R_2 = R$, and input current drawn by the OP AMP is negligible.

- Q.10.** If charge on the capacitor is reset to zero, prove that the output voltage ' V_O ' in the circuit given in Fig. 5 below, is expressed by $V_O(t) = -\frac{1}{RC} \int_0^t (V_1 + V_2) dt$

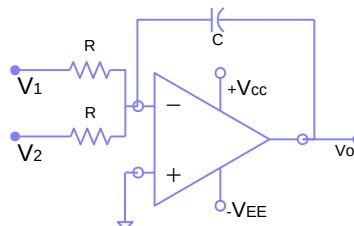


Fig. 5

- Q.11.** Find the frequency for which the amplifier gain V_o/V_s in Fig. 6 is minimum. What is the value of the minimum gain? Assume the op-amp to be ideal. Take $R=1k\Omega$ and $C=\pi\mu F$.

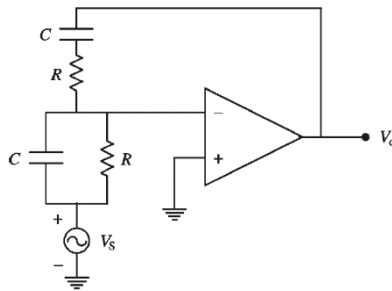


Fig. 6

- Q.12.** Full scale deflection current for dc microammeter used in the Fig. 7 is $50\mu A$ and its internal resistance is $2k\Omega$. A dc voltmeter of 0-10V is to be constructed using ammeter circuit shown. Find the value of R_1 . Which of the two terminals, + or -, of the microammeter is required to be grounded?

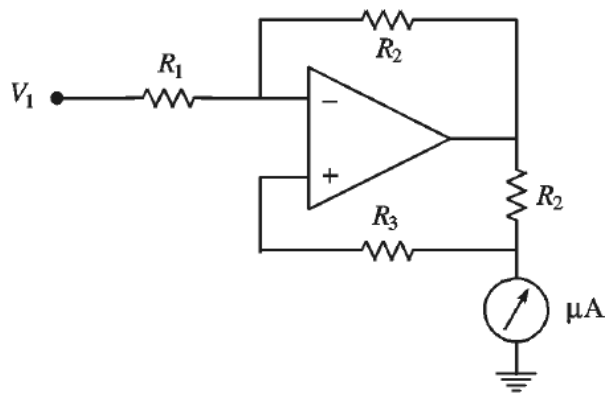


Fig. 7

- Q.13.** Using a 555 timer, design an astable multivibrator of frequency 250Hz and duty cycle „D0“% (Where D is the last digit of your ID number. For example if your number is 20XXXXXX012H, the duty cycle should be 20%. If your ID number ends with a zero, the duty cycle has to be 25%).

- Q.14.** Prove that the circuit given in Fig. 8 below converts change in transducer resistance to voltage where offset voltage is zeroed by potentiometer

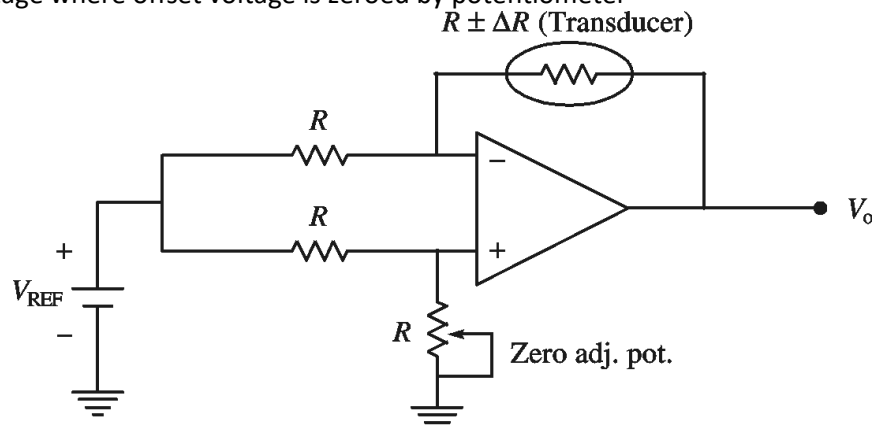


Fig. 8

Q.15. Find out the output voltage in the Fig. 9 below. Given that $+V=5V$, $V_Z = 3.3V$, $R=220\Omega$. For Fig.(a), the value of $R_F = 20k\Omega$, and $R_I = 10k\Omega$, and for Fig.(b) $R_F = R_I = 10k\Omega$

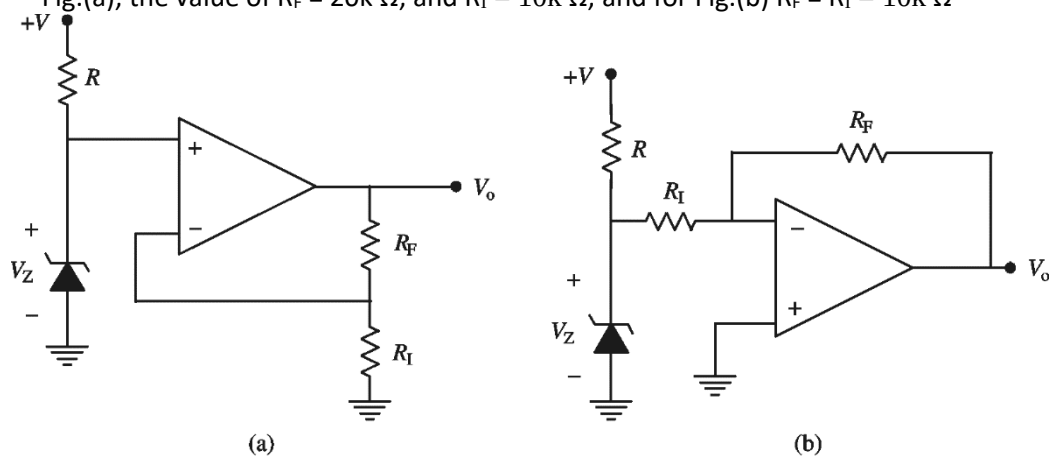


Fig. 9