

Assignment-3

① A 1- ϕ transmission line has a resistance of 0.2Ω and an inductive reactance of 0.4Ω . find the voltage at the sending end to give 500 kVA at 2 kV at receiving end at load power factors of

- (i) Unity
- (ii) 0.707 lagging.

Illustrate with suitable phasor diagrams.

② A 3- ϕ transmission line has the following data

Resistance of each conductor = 20Ω

Inductive reactance of each conductor = 40Ω

Capacitive susceptance to neutral = 0.0004 S .

Load at the receiving end = 12,500 kVA at 0.8 lagging

Voltage at receiving end = 66 kV.

Find

(a) Sending end voltage and current

(b) Sending end power factor

(c) efficiency (d) Regulation of the line.

Use nominal-T method and draw

the phasor diagram.

3. A 50 Hz, 3- ϕ transmission line of length 30 km has a total series impedance of $(40 + j125) \Omega$ and shunt admittance of 10^{-3} mho. Find the sending end voltage. Use nominal π representation.

4. Determine the corona loss for 3- ϕ line operating at 110 kV which has conductors of 1.25 cm dia arranged in a 3.05 m delta configuration. Assume polished wires and air density factor of 1.07.

5. A, 3- ϕ transmission line, 160 km long has the following constants:

Resistance per phase per km = 0.2Ω

Reactance per phase per km = 0.3127Ω

Shunt admittance per phase per km = $1.875 \times 10^{-6} S$

Determine the sending end voltage and current by rigorous method when the line is delivering a load of 25 MVA at 0.8 power factor lagging. The receiving end voltage is kept constant at 110 kV.