

Name of the Student Prashant Scholar Number 221190124

MAULANA AZAD NATIONAL INSTITUTE OF TECHNOLOGY BHOPAL
DEPARTMENT OF ELECTRICAL ENGINEERING
MID TERM EXAM MARCH 2024

Course: B. Tech

Semester: IV

Subject Name: Electronic Devices and Circuits

Subject Code: EE 223

Time Duration: 1 Hour 30 Minutes

Maximum Marks: 20

S No	Question	Marks	CO
1.(a)	Identify and justify the application of Op-Amp, if inverting amplifier is modified by (i) R_i is replaced by C and R_o is replaced by C.	2.5	CO2
1.(b)	Realize an Op-Amp circuit to solve a differential equation of $\frac{d^2v}{dt^2} = -40 \frac{dv}{dt} - 100v + X$ (X = Last two digits of Sch. Number)	2.5	CO3
2.(a)	How feedback system affects the performance of Op-Amp? Design circuit for generation of 650 Hz sinusoidal waveform using Wein-bridge oscillator. Assume $C = 0.05 \mu F$ and $R_1 = 10 k\Omega$	2.5	CO3
2.(b)	Estimate the ON time, OFF time and free running frequency of output wave form, if 555 timer is working in astable mode. Given $V_{cc} = 5 V$, $R_A = 2.2 k\Omega$, $R_B = 3.9 k\Omega$ and $C = 0.1 \mu F$.	2.5	CO4
3.	How half adder and half subtractor circuit can be implemented using logic gates with solution of K- Maps ?	05	CO3
4.	Design logic gate circuit with K- Maps solution for operation of BCD to 7 segment decoder to display "7". (Assume common anode display) (i) Using IC (ii) Using basic logic gates	05	CO4